



GN010 Application Note

EZDrive® Power Stage Solution for GaN Systems' GaN Transistor


June 2020

GaN Systems Inc.




- Introduction
- GaN discrete versus integrated options
- GaN Systems' solution: EZDrive circuit
- EZDrive circuit verification
- Summary

Using the controller/driver to drive GaN

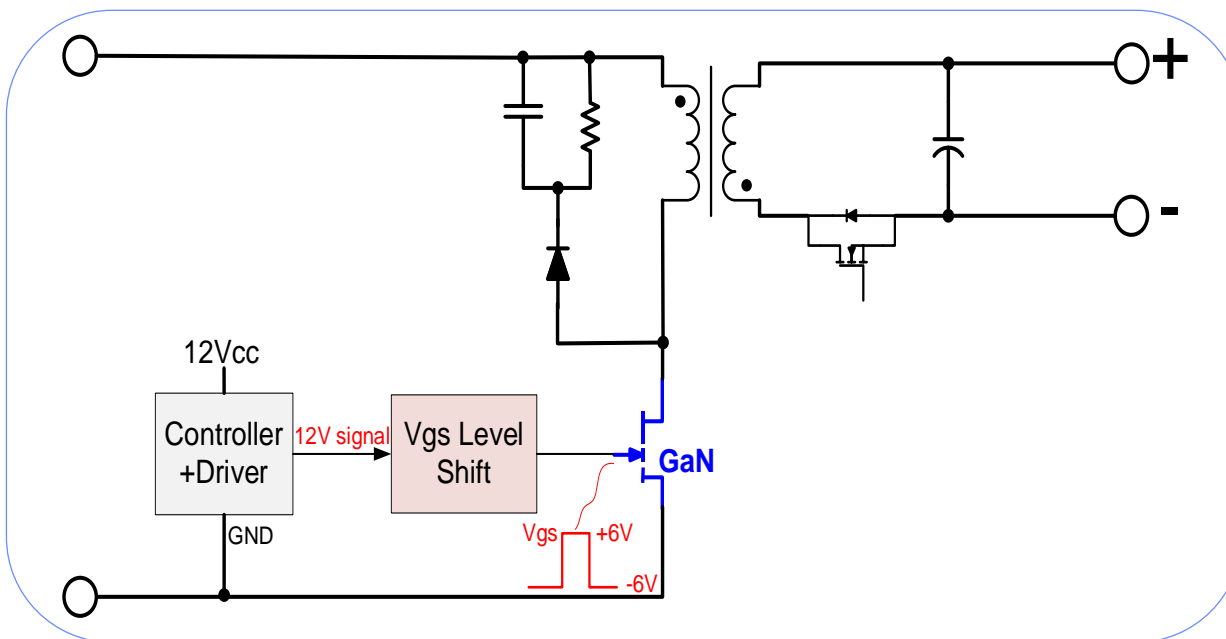

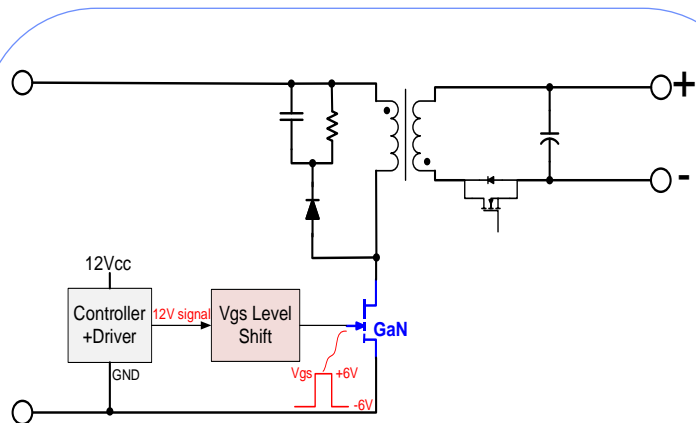
- Controllers with Drive have an output signal of 12V
- The GaN transistor needs +6V for turn on
- Additional V_{gs} level shift is needed



- Controllers with Drive have an output signal of 12V
- GaN transistors need +6V for turn on
- Additional Vgs level shift is needed

Integrated


Monolithic-Integrated GaN

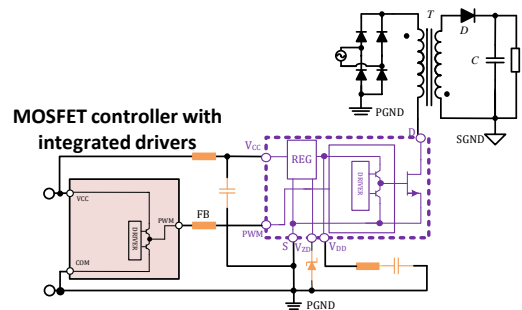

- Internal regulator to convert 12V/0V to +6V/0V

Discrete

GaN Systems EZDrive Circuit + GaN

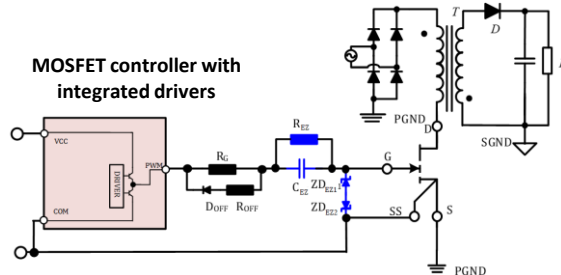


- Level shift circuit to convert 12V/0V to +6V/-6V

- Introduction
- GaN discrete versus integrated options
- GaN Systems' solution: EZDrive circuit
- EZDrive circuit verification
- Summary

GaN discrete versus integrated design


GaN Systems EZDrive Solution

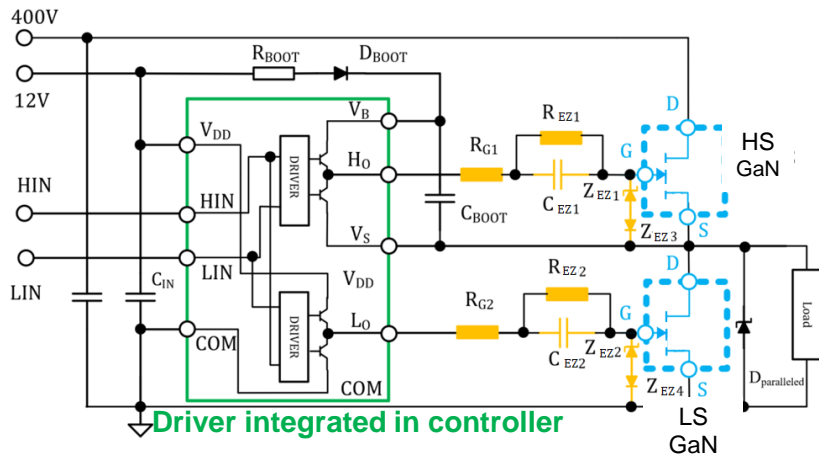

Fewest circuit blocks + standard componentry
(cost effective: same number of passive components, no extra driver)

Control Turn-on, turn-off, negative drive
(optimized EMI and efficiency)

Monolithic-integrated Solution

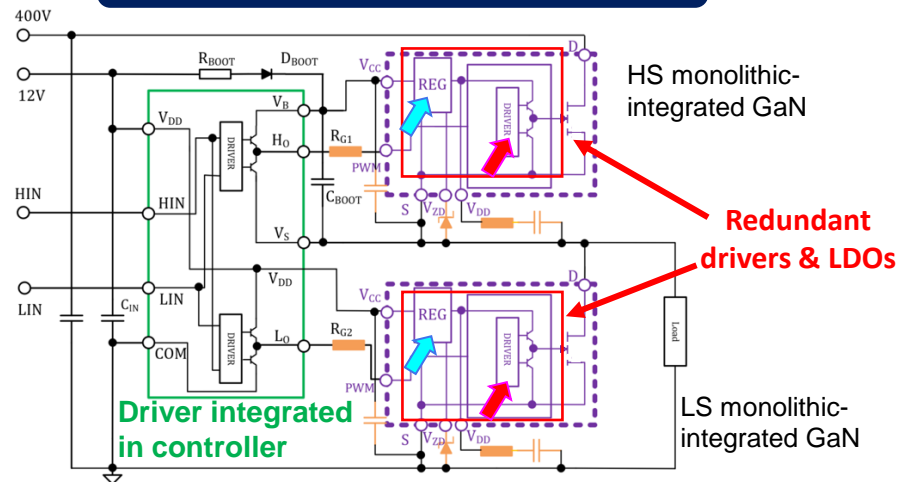

Integrated = 2 extra Drivers + 2 extra LDOs
(higher cost and complexity)

Control of turn-on only
(sub-optimal performance)





Discrete solution is lower in cost and better for EMI and efficiency

GaN discrete versus integrated T_{ON}/T_{OFF} control



Monolithic-integrated GaN

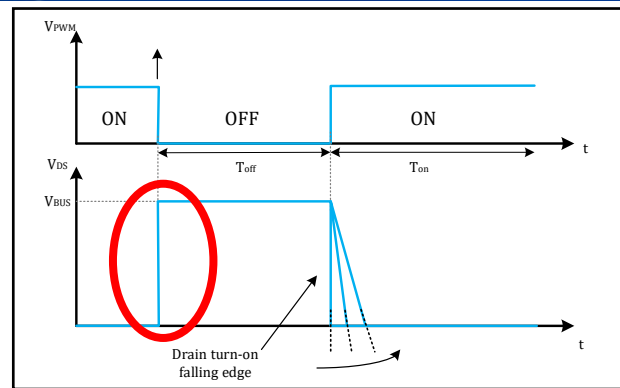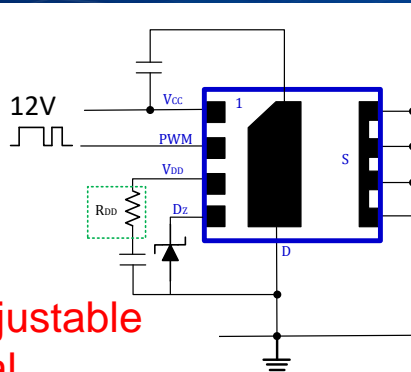- Drain turn-off rising edge NOT adjustable
- Limits design flexibility, not optimal



Discrete GaN with EZDrive circuit

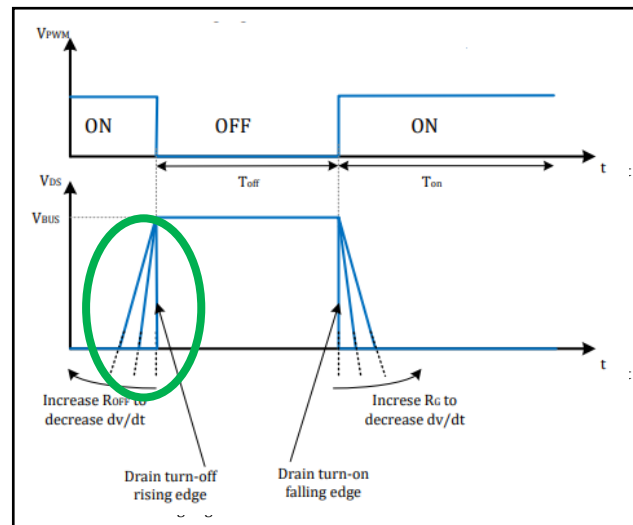
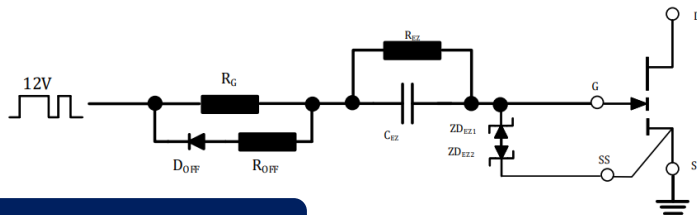
- Drain turn-off rising **AND** turn-on falling edge adjustable
- Optimized EMI and efficiency



- Introduction
- GaN discrete versus integrated options
- GaN Systems' solution: EZDrive circuit
- EZDrive circuit verification
- Summary


GaN Systems' **EZDrive** circuit is a low cost, easy way to implement a **GaN driving circuit**.

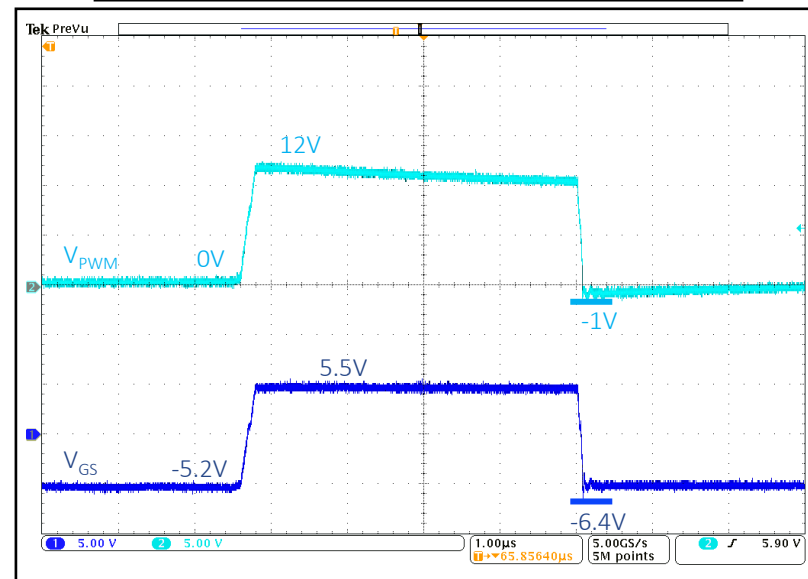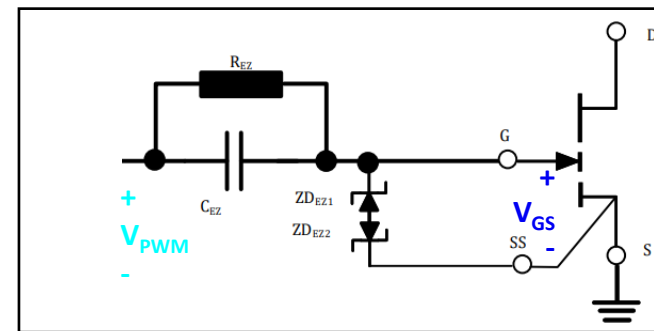- Enables 12V driver to drive 6V GaN
- Level shift circuit composed of 4 components
- Turn ON / OFF slew rate is controllable with external resistors R_g to optimize EMI
- Adjustable to any power level, any frequency, and any standard controller/driver
- Applies to any controllers with single, dual, or high-side/low-side drivers




Operation modes of EZDrive solution


Mode 1: C_{BOOT} Charging (HS GaN: off; LS GaN: on)

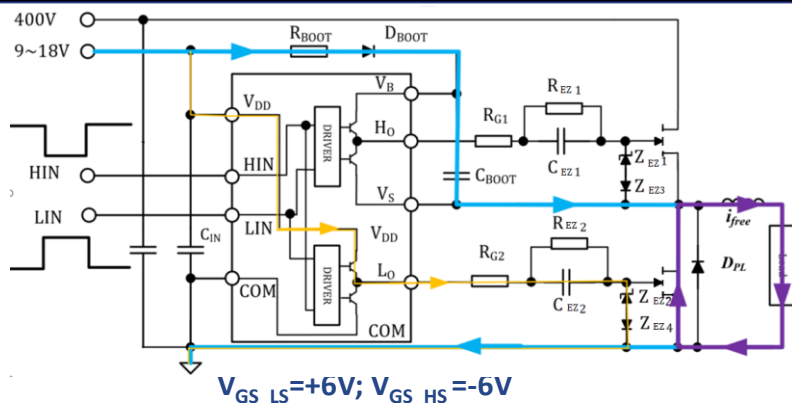

Mode 2: C_{BOOT} Charging (HS GaN: off; LS GaN: off)

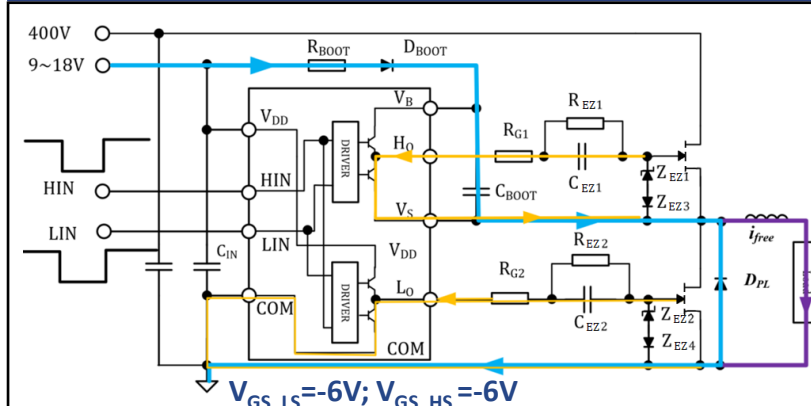

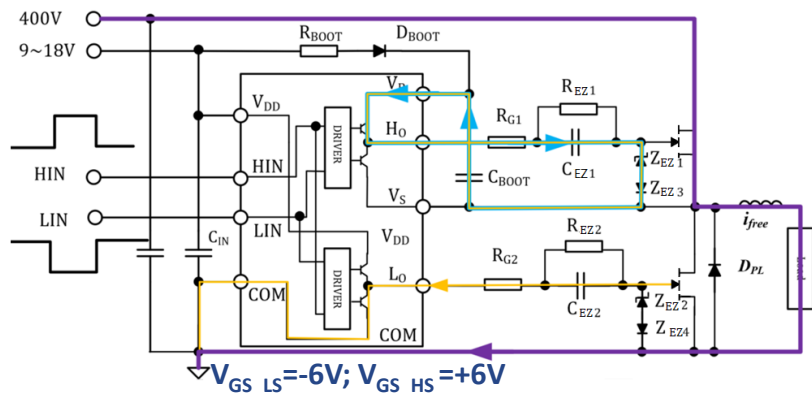Mode 3: C_{BOOT} Discharging (HS GaN: on; LS GaN: off)




- EZDrive operation modes in half bridge are **similar to** conventional non-isolated Bootstrap high side/low side driver
- Allows **wide controller bias input voltage range** (9~18V)

EZDrive circuit application examples


Typical applications with the EZDrive circuit

- Flyback
- Half Bridge
- Boost PFC

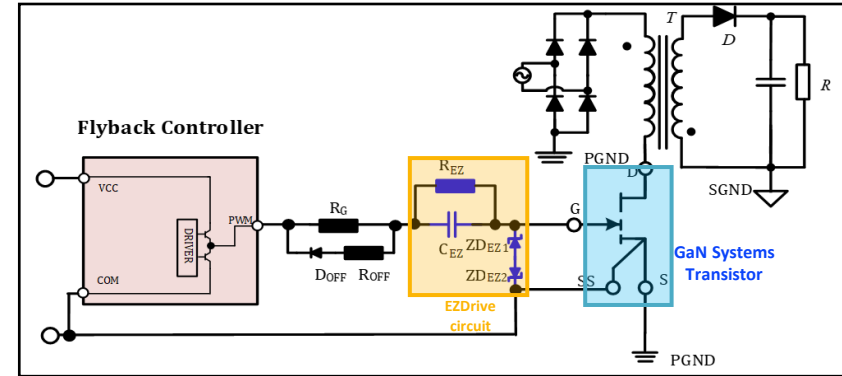
Solution = GaN discrete + EZDrive circuit + Controller



Flyback with EZDrive solution

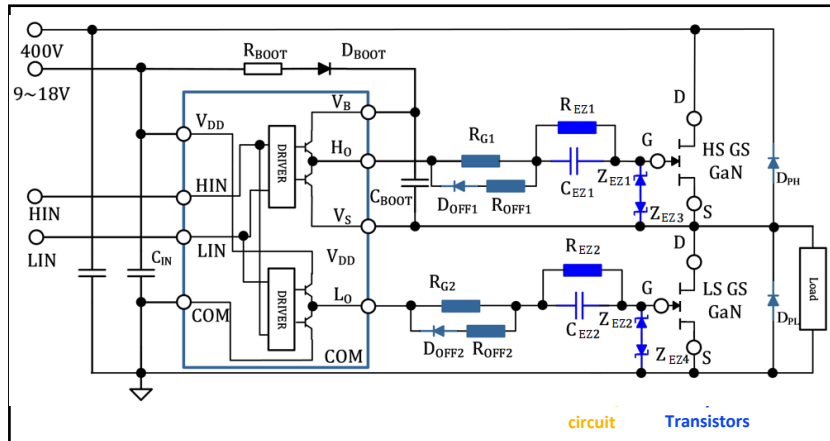


Half Bridge with EZDrive solution

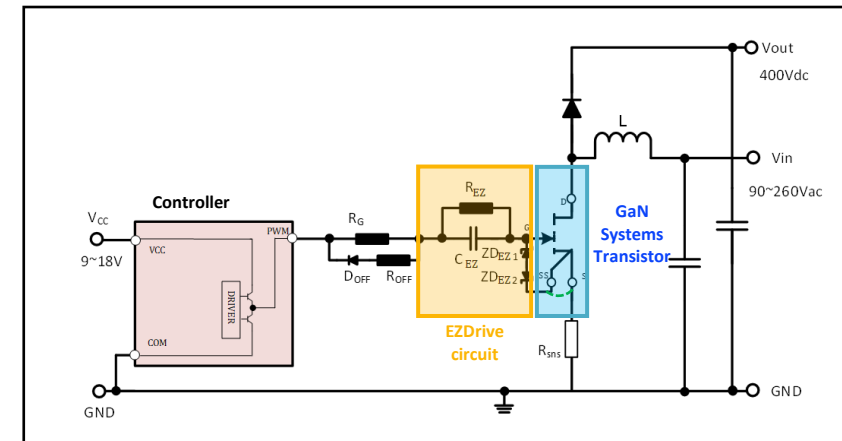

Boost PFC with EZDrive solution

Flyback EZDrive circuit

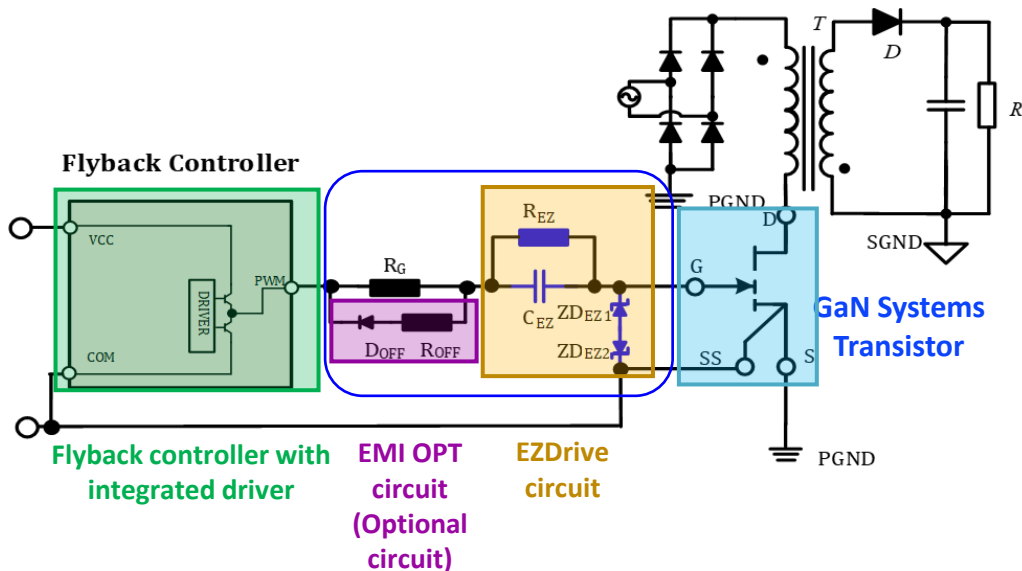- Flyback controller examples include NCP1342 and NCP1250
- The circuit and tables show recommended values for the Flyback EZDrive circuit
 - As an option, similar to silicon MOSFET-based designs, efficiency and EMI can be further optimized with the labeled "optional circuit"



EZDrive Circuit


Symbol	Value	Footprint	Function
R_{EZ}	$\sim 10 \text{ k}\Omega$	0402 / 0603	Keep the driving voltage
C_{EZ}	$\sim 47 \text{ nF}$	0402 / 0603	Hold negative voltage for turning off
Z_{EZ1}	5.6 V Zener	SOD923F / 0603	Clamp the positive gate voltage
Z_{EZ2}	9.1 V Zener	SOD923F / 0603	Clamp the negative gate voltage

Efficiency and EMI Optimization Circuit (Optional)

Symbol	Value	Rec. Footprint	Function
D_{OFF}	20V Diode 1A	SOD923F / 0603	Enable independent turn-off speed control
R_{OFF}	0Ω	0402 / 0603	Control turn-off speed

Half Bridge EZDrive circuit

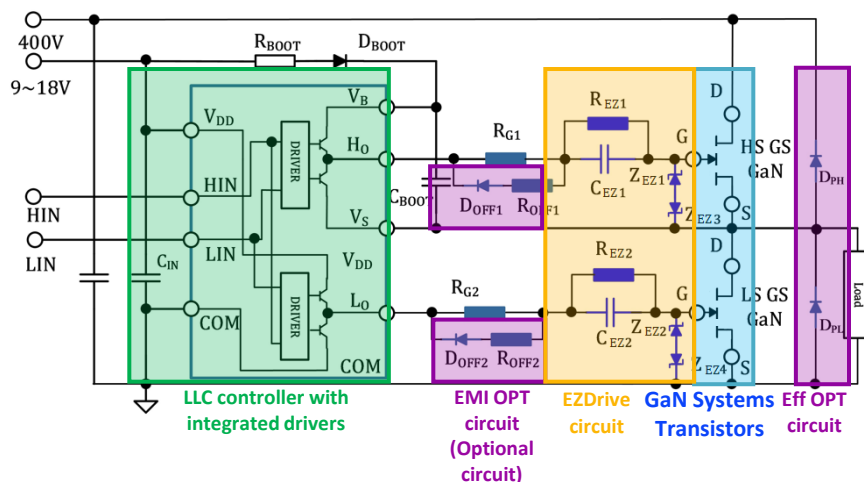- Half Bridge controller examples include NCP1399 and NCP13992
- The circuit and tables show recommended values for the Half Bridge EZDrive circuit
 - As an option, similar to silicon MOSFET-based designs, efficiency and EMI can be further optimized with the labeled “optional circuit”



EZDrive Circuit


Symbol	Rec. Value	Rec. Footprint	Function
$R_{EZ1,2}$	$\sim 10 \text{ k}\Omega$	0402 / 0603	Keep the driving voltage
$C_{EZ1,2}$	$\sim 47 \text{ nF}$	0402 / 0603	Hold negative voltage for turning off
$Z_{EZ1,2}$	5.6 V Zener	SOD923F / 0603	Clamp the positive gate voltage
$Z_{EZ3,4}$	9.1 V Zener	SOD923F / 0603	Clamp the negative gate voltage

Efficiency and EMI Optimization Circuit

Symbol	Rec. Value	Rec. Footprint	Function
$D_{OFF1,2}$	20V DIODE 1A	SOD923F / 0603	Optional for Enabling independent turn-off speed control
$R_{OFF1,2}$	0 Ω	0402 / 0603	Optional for Controlling turn-off speed
D_{PL}	600V FRD 1A	SOD123F / SMA	Avoid C_{BOOT} overcharging, for reduced low side P_{DT} (Note 1)
D_{PH}	600V FRD 1A	SOD123F / SMA	Optional for reduced high side P_{DT} (Note 1)

Note 1: D_{PH} and D_{PL} are not required if the controller has an internal Sync Boot function to regulate bootstrap voltage

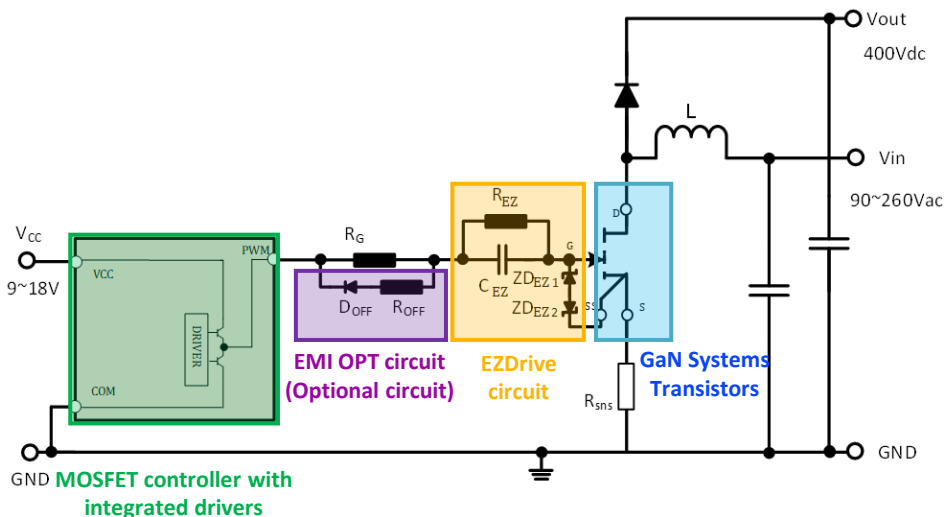- Boost PFC controller examples include NCP1616, NCP1615, and L6562A
- The circuit and tables show recommended values for the Boost PFC EZDrive circuit
 - As an option, similar to silicon MOSFET-based designs, efficiency and EMI can be further optimized with the labeled "optional circuit"



EZDrive Circuit


Symbol	Rec. Value	Rec. Footprint	Function
R_{EZ}	$\sim 10 \text{ k}\Omega$	0402 / 0603	Keep the driving voltage
C_{EZ}	$\sim 47 \text{ nF}$	0402 / 0603	Hold negative voltage for turning off
Z_{EZ1}	5.6 V Zener	SOD923F / 0603	Clamp the positive gate voltage
Z_{EZ2}	9.1 V Zener	SOD923F / 0603	Clamp the negative gate voltage

Efficiency and EMI Optimization Circuit (Optional)


Symb ol	Rec. Value	Rec. Footprint	Function
D_{OFF}	20V DIODE 1A	SOD923F / 0603	Enable independent turn-off speed control
R_{OFF}	0 Ω	0402 / 0603	Control turn-off speed

- Introduction
- GaN discrete versus integrated options
- GaN Systems' solution: EZDrive circuit
- EZDrive circuit verification
- Summary

Flyback topology verification test setup

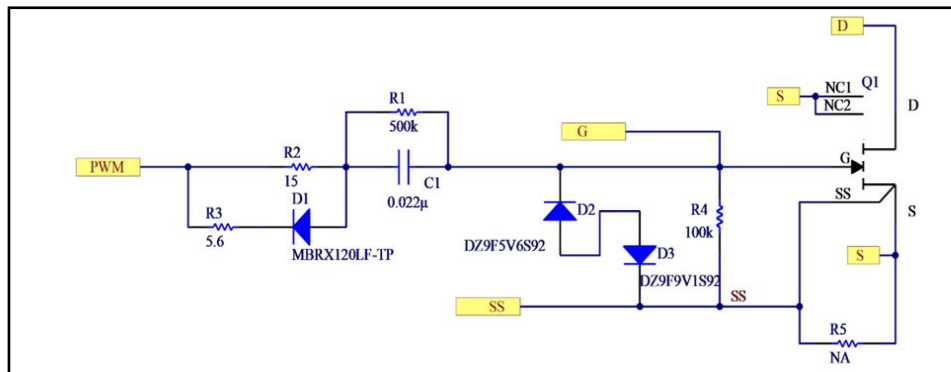

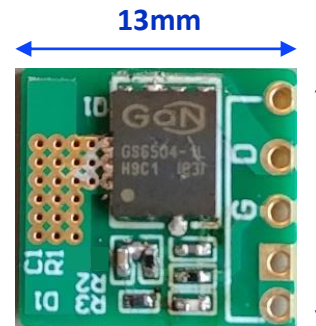Flyback EZDrive circuit with Efficiency optimization





Front side




Back side

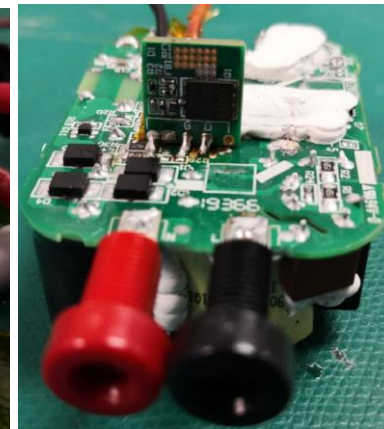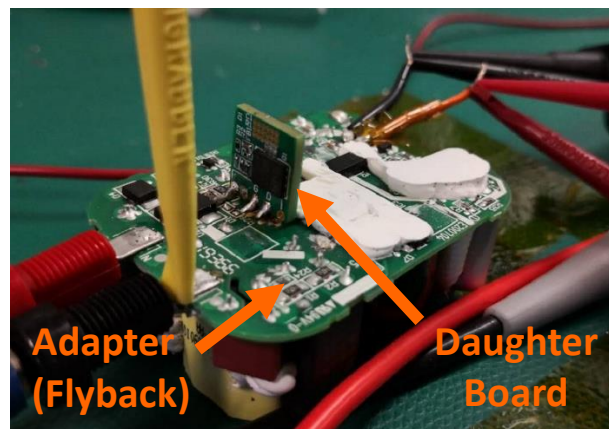- Populate GaN daughter card with GaN transistor and EZDrive components
- Modify off-the-shelf adapter
- Solder in GaN + EZDrive circuit daughter board




Flyback topology verification data

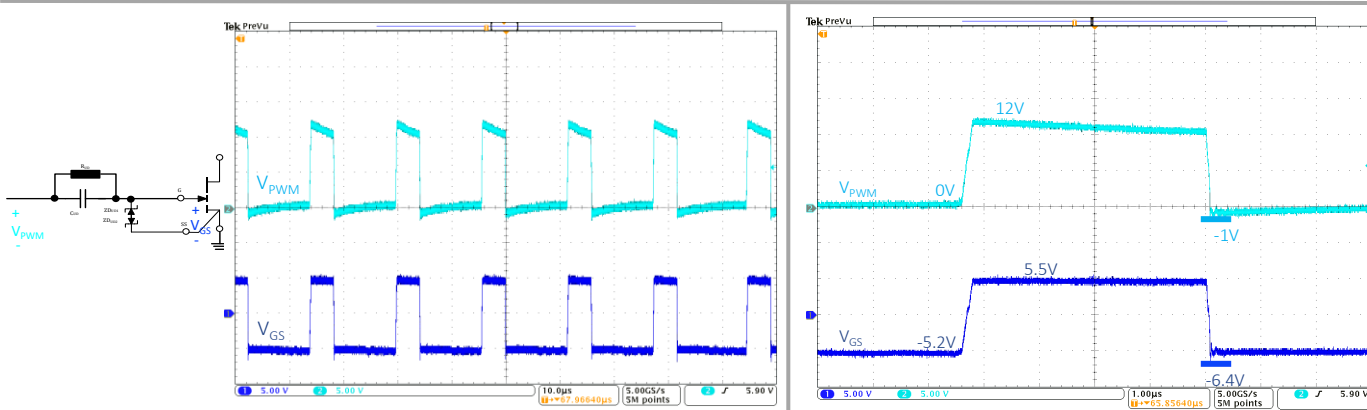EZDrive Waveforms (V_{PWM} & V_{GS}) @ full load (18V/1.67A output)



Temp. Distribution @ full Load

115Vac input at 18V/1.67A output

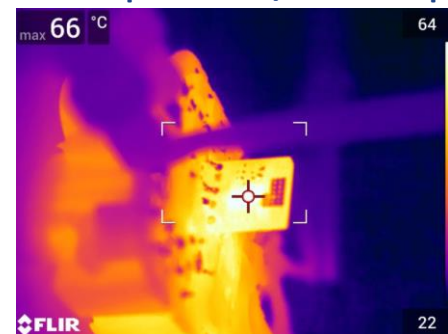



Skip Mode Operation @ 5% Loads

Skip frequency: 1.2KHZ

Pulse frequency: 22KHZ

Skip frequency: 1.6KHZ


Pulse frequency: 22KHZ

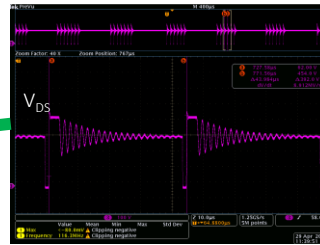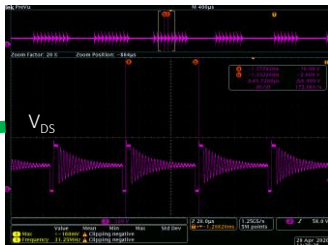

115Vac input, Average frequency=13KHZ

230Vac input, Average frequency=8KHZ

230Vac input at 18V/1.67A output

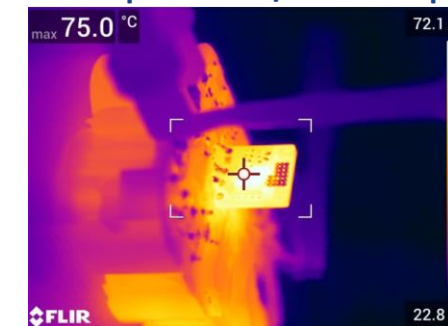

- No overshoot/undershoot on V_{GS} in all operating conditions
- Low operating temperatures


Flyback topology verification data

Temp. Distribution@ full Load


115Vac input at
18V/1.67A output



230Vac input at
18V/1.67A output

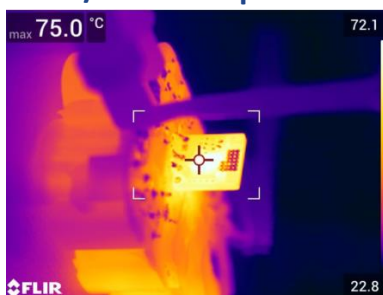

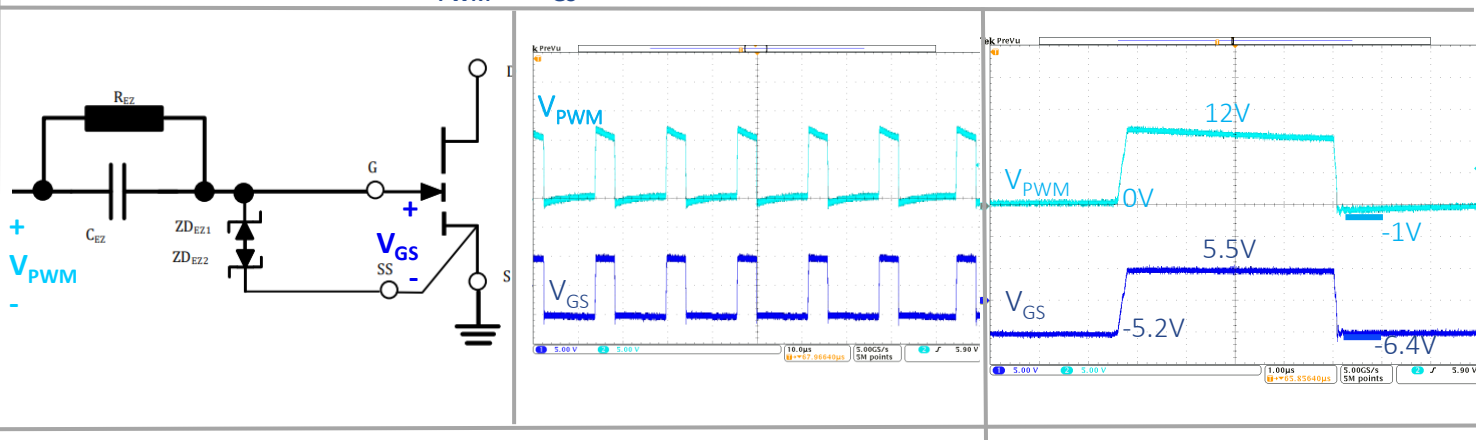
EZDrive Waveforms (V_{PWM} & V_{GS}) @ full load (18V/1.67A output)



Skip Mode Operation @ 5% Loads

Skip frequency:1.2KHZ


Pulse frequency:22KHZ

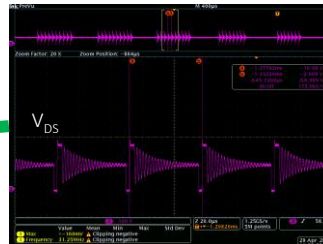

115Vac input, Average frequency=13KHz

Skip frequency:1.6KHZ


Pulse frequency:22KHZ

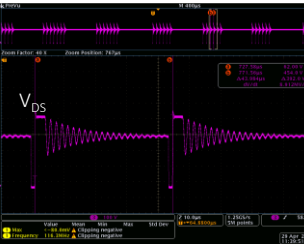

230Vac input, Average frequency=8KHz

- No overshoot/undershoot on V_{GS} in all operating conditions
- Low operating temperatures

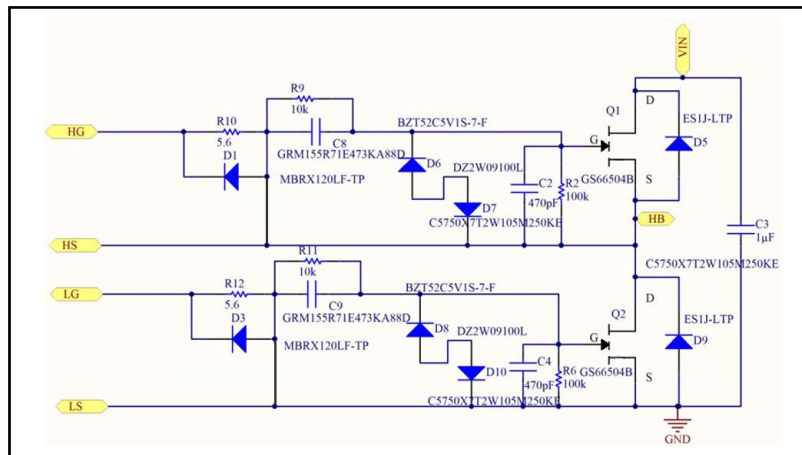
Half Bridge LLC topology verification setup




Half Bridge LLC EZDrive schematic



Test board (Top View)

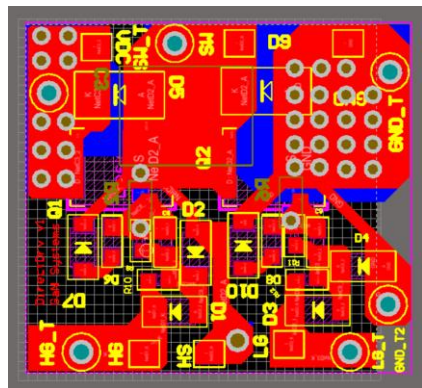

Half Bridge EZDrive layout

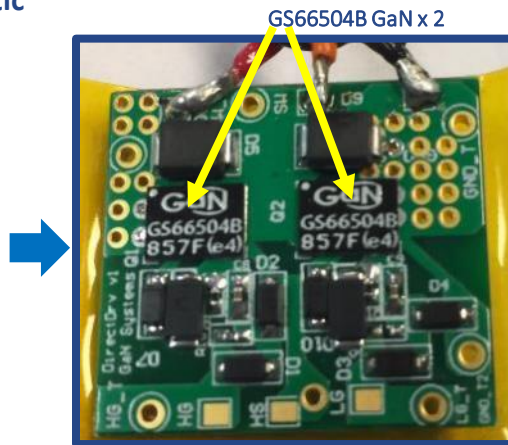


EZDrive Daughter Card



Test board (Bottom View)

Half Bridge LLC verification data

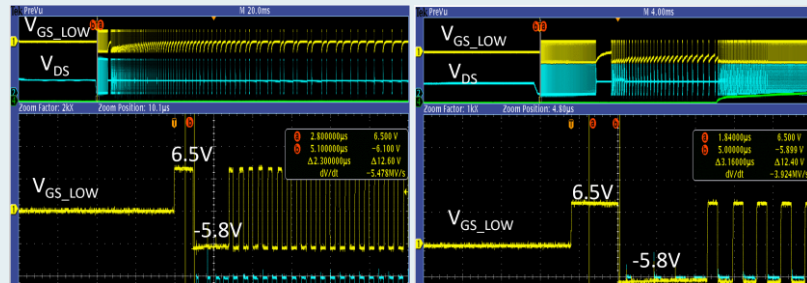

@ no load ($I_{out}=0A$)

@ full load ($I_{out}=20A$)


Start-up Process



0A to 20A

20A to 0A


Load Step Change

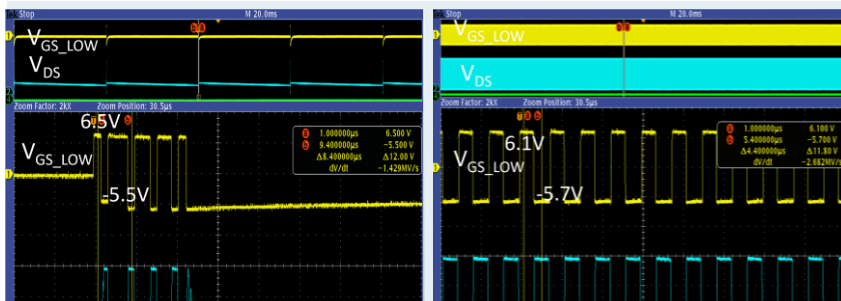

@ no load ($I_{out}=0A$)

@ full load ($I_{out}=20A$)

Static Operation

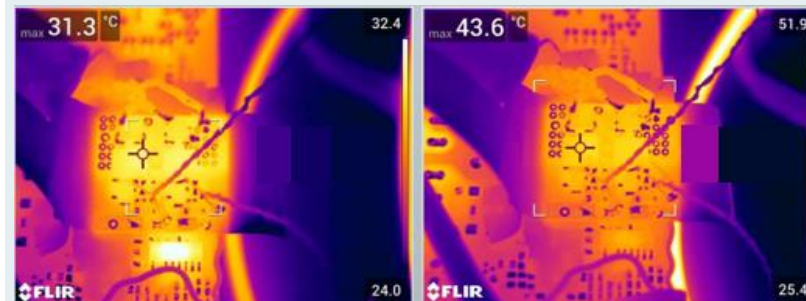

@ half load (10A)


@ full load (20A)

Temperature Distribution


- No overshoot/undershoot on V_{GS} & V_{DS} in all operating conditions
- Low operating temperatures

Boost PFC topology verification test setup

EZDrive PFC daughter card schematic

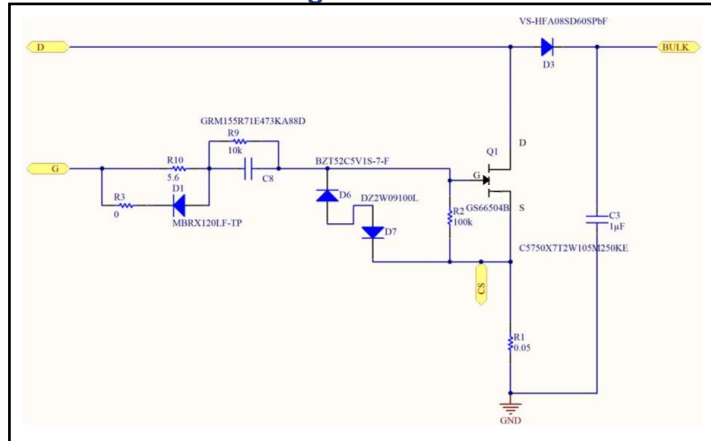

EZDrive PFC daughter card

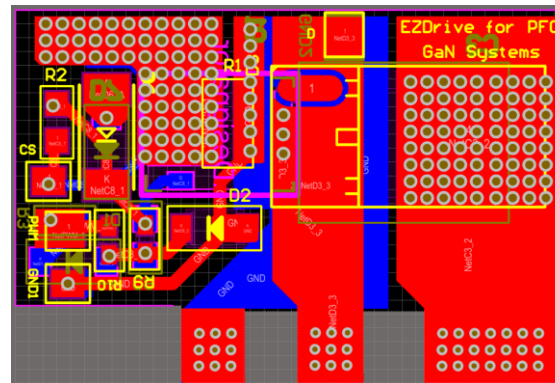

PFC with transition-mode controller L6562A (Top View)



PFC with transition-mode controller L6562A (Side View)



650V 15A GaN Transistor: GS66504B




top



bottom

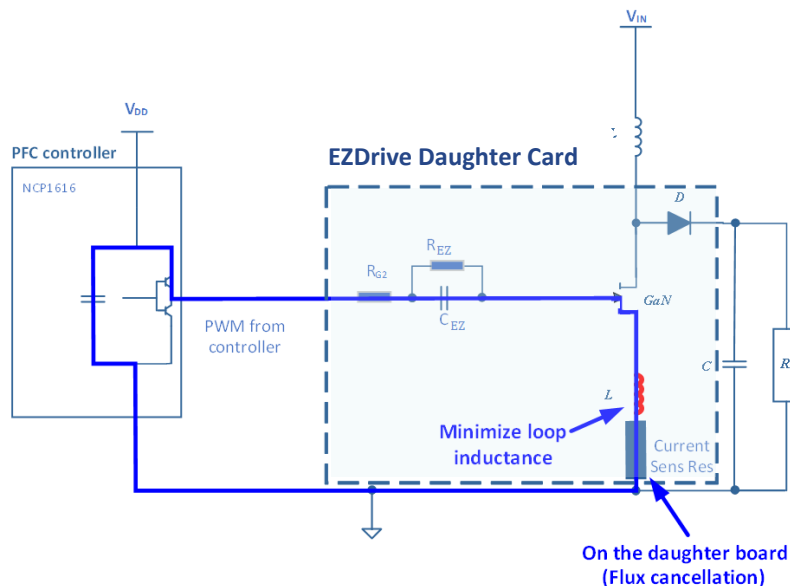
- For power greater than 65W, a daughter card is typically used in the design for improved thermal performance
- The table below provides layout recommendations




Layout recommendations	Objectives
<ul style="list-style-type: none">• Shorten the trace length between the sensing resistor and Power GND	Reduce trace inductance
<ul style="list-style-type: none">• Put the sensing resistor and GaN back-to-back on the 2-layer board• Using a 4-layer PCB will further reduce the common inductance and result in improved thermal performance	Flux cancellation → reduce the mutual inductance
<ul style="list-style-type: none">• Optionally use SMD current sensing resistor instead of THT	Reduce the parasitic inductance

Boost PFC topology verification data


Start-up Process

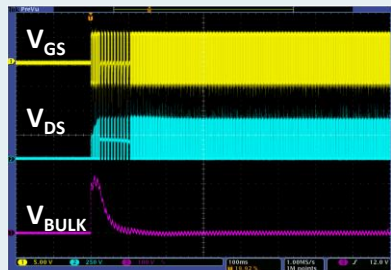


@ 110Vac & full load (400V, 0.5A)

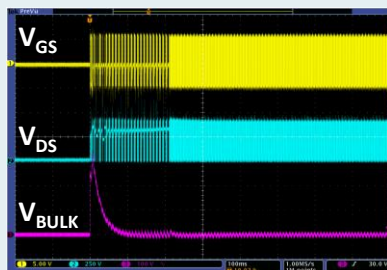

@ 220Vac & full load (400V, 0.5A)

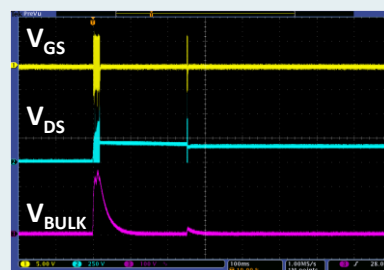


@ 110Vac & no load (400V, 0A)

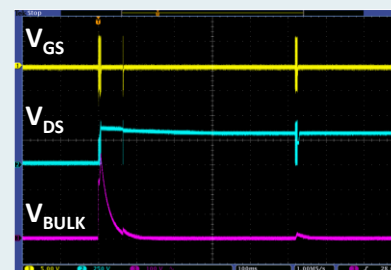


@ 220Vac & no load (400V, 0A)

Static Operation

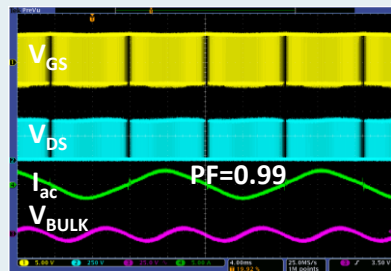


@ 110Vac & full load (400V, 0.5A)

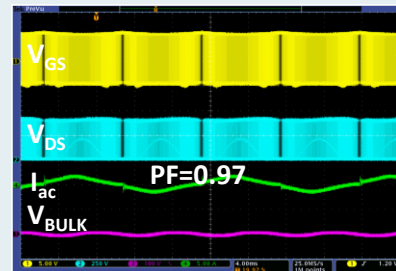


@ 220Vac & full load (400V, 0.5A)

Load Step Change

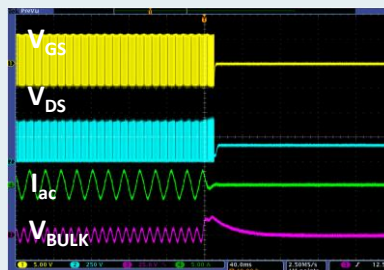

Full load to no load (0.5A to 0A)

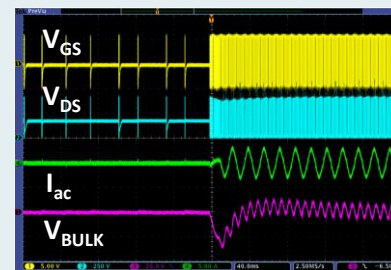

No load to full load (0A to 0.5A)

- No overshoot/undershoot on V_{GS} & V_{DS} in all operating conditions

- Introduction
- GaN discrete versus integrated options
- GaN Systems' solution: EZDrive circuit
- EZDrive circuit verification
- **Summary**

Application Considerations	Silicon MOSFETS	GaN Systems EZDrive circuit	Monolithic GaN + driver
Total BoM Cost	✓	✓	✗
Choice of devices to optimize design	✓	✓	✗
Use controller driver, eliminate redundancy	✓	✓	✗
EMI control	✓	✓	✗
Power density	✗	✓	✓



GaN Systems **EZDrive** circuit is a **low cost**, easy way to implement a GaN driving circuit with a standard MOSFET controller with integrated driver

- GaN transistor information

- <https://gansystems.com/gan-transistors/>



- EZDrive evaluation kit

- <https://gansystems.com/evaluation-boards/gs65011-evbez/>



- Technical article

- <https://gansystems.com/wp-content/uploads/2020/01/Using-Mosfet-Controllers-to-Drive-GaN-EHEMTs.pdf>

Bodo's Power Systems®
Using MOSFET Controllers
to Drive GaN E-HEMTs

- Reference Designs

- Contact us for information, samples and designs





GaN Systems

www.gansystems.com . North America . Europe . Asia